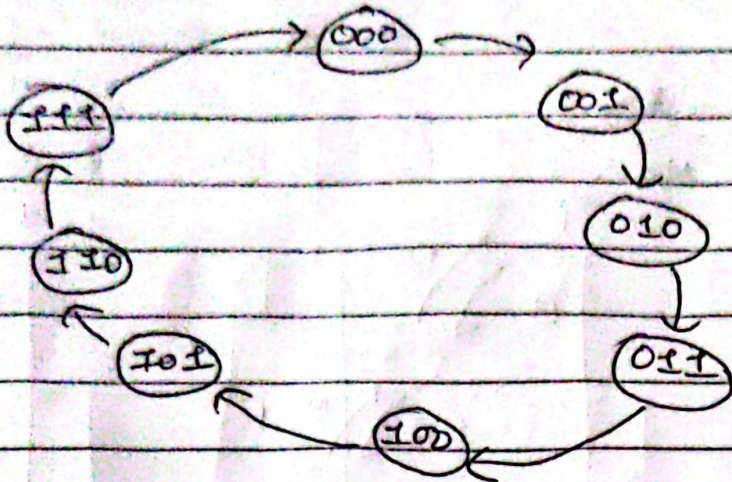


Design octal counter (mod-8) asynchronous

⇒ Solution :-



Logic high
= 1

