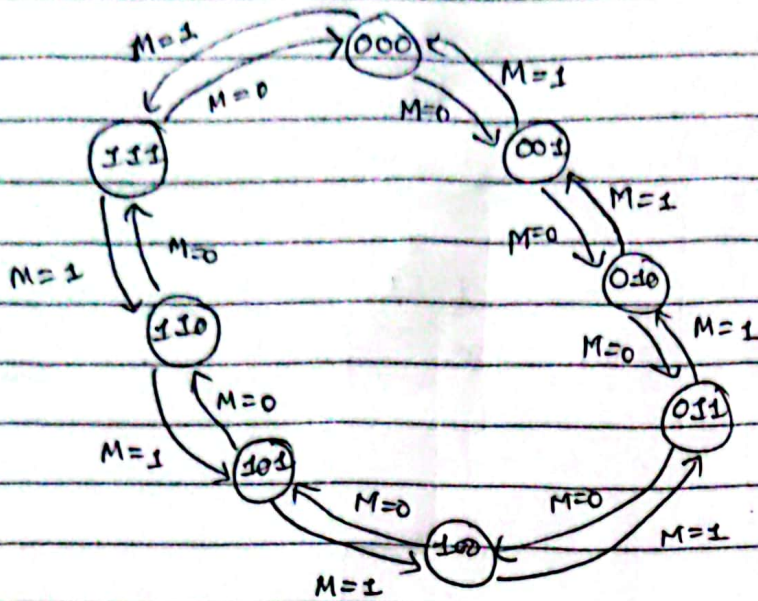


* Design up/down counter (synchronous)

⇒ Solution:-

1) State Table:-

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0



2) State Diagram

Mode	Present state			Next state			Flip Flops		
	Q_2	Q_1	Q_0	Q_2'	Q_1'	Q_0'	T_2	T_1	T_0
0	0	0	0	0	0	1	0	0	1
0	0	0	1	0	1	0	0	1	1
0	0	1	0	0	1	1	0	0	1
0	0	1	1	1	0	0	1	1	1
0	1	0	0	1	0	1	0	0	1
0	1	0	1	1	1	0	0	1	1
0	1	1	0	1	1	1	0	0	1
0	1	1	1	0	0	0	1	1	1
1	0	0	0	1	1	1	1	1	1
1	0	0	1	0	0	0	0	0	1
1	0	1	0	0	0	1	0	1	1
1	0	1	1	0	1	0	0	0	1
1	1	0	0	0	1	1	1	1	1
1	1	0	1	1	0	0	0	0	1
1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	1	0	0	0	1

T_2

$M Q_2$	$Q_1 Q_0$			
	00	01	11	10
00			1	
01			1	
11	1			
10	1			

$$T_2 = \overline{M} Q_1 Q_0 + M \overline{Q}_1 \overline{Q}_0$$

T_1

$M Q_2$	$Q_1 Q_0$			
	00	01	11	10
00		1	1	
01		1	1	
11	1			1
10	1			1

$$T_1 = \overline{M} Q_0 + M \overline{Q}_0$$

T_0

$M Q_2$	$Q_1 Q_0$			
	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$T_0 = 1$$

